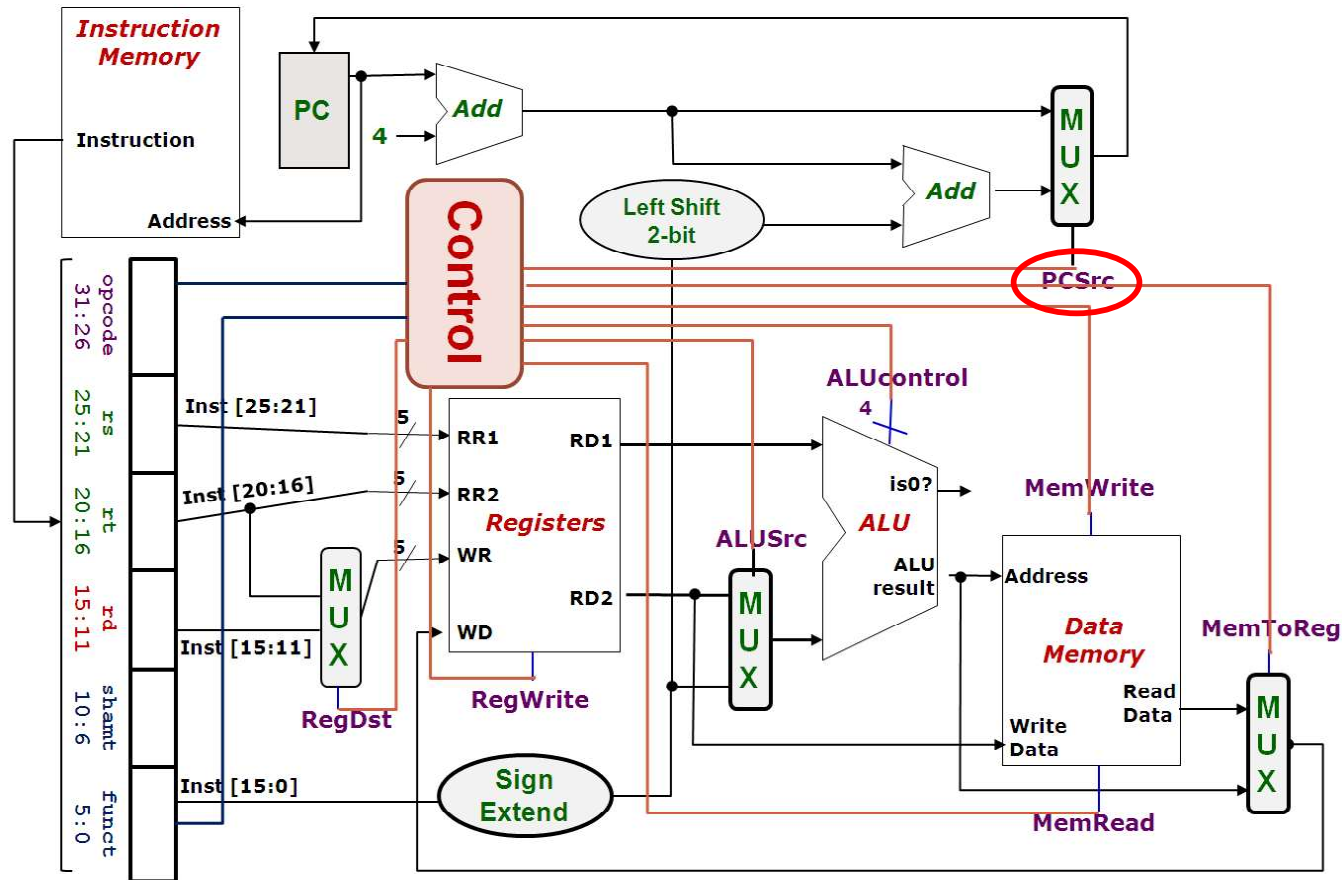


## 4. Control Signal: PCSrc (1/2)


- The "isZero?" signal from the ALU gives us the actual branch outcome (taken/not taken)
- **Idea:** “If instruction is a branch **AND** taken, then...”



## 5. One Bit At A Time (Aha!)

- Can you see how the **ALUcontrol** (4-bit) signal controls the ALU?
  - Note: implementation for **slt** not shown

ALUcontrol			Function
Ainvert	Binvert	Operation	
0	0	00	AND
0	0	01	OR
0	0	10	add
0	1	10	subtract
0	1	11	slt
1	1	00	NOR

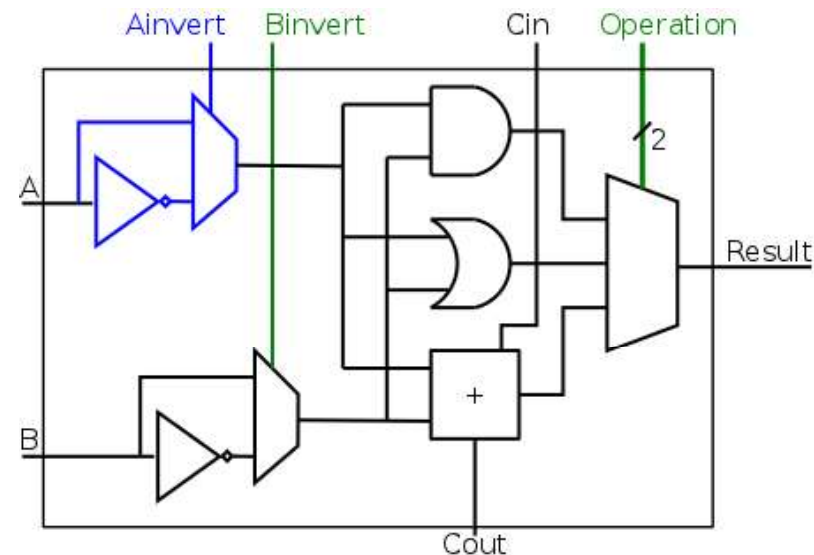

## 5. Generating ALUcontrol Signal

Opcode	ALUop	Instruction Operation	Funct field	ALU action	ALU control
lw	00	load word	xxxxxx	add	0010
sw	00	store word	xxxxxx	add	0010
beq	01	branch equal	xxxxxx	subtract	0110
R-type	10	add	10 0000	add	0010
R-type	10	subtract	10 0010	subtract	0110
R-type	10	AND	10 0100	AND	0000
R-type	10	OR	10 0101	OR	0001
R-type	10	set on less than	10 1010	set on less than	0111

Instruction Type	ALUop
lw / sw	00
beq	01
R-type	10

ALUcontrol	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	slt
1100	NOR

Generation of 2-bit **ALUop** signal will be discussed later



## 5. Design of ALU Control Unit (1/2)

- Input: 6-bit **Func** field and 2-bit **ALUop**
- Output: 4-bit **ALUcontrol**
- Find the simplified expressions

ALUcontrol3 = 0

ALUcontrol2 = ?


ALUop0 + ALUop1 · F1

	ALUop		Func Field ( F[5:0] == Inst[5:0] )						ALU control
	MSB	LSB	F5	F4	F3	F2	F1	F0	
lw	0	0	X	X	X	X	X	X	0 0 1 0
sw	0	0	X	X	X	X	X	X	0 0 1 0
beq	<del>0</del> X	1	X	X	X	X	X	X	0 1 1 0
add	1	<del>0</del> X	<del>1</del> X	<del>0</del> X	0	0	0	0	0 0 1 0
sub	1	<del>0</del> X	<del>1</del> X	<del>0</del> X	0	0	1	0	0 1 1 0
and	1	<del>0</del> X	<del>1</del> X	<del>0</del> X	0	1	0	0	0 0 0 0
or	1	<del>0</del> X	<del>1</del> X	<del>0</del> X	0	1	0	1	0 0 0 1
slt	1	<del>0</del> X	<del>1</del> X	<del>0</del> X	1	0	1	0	0 1 1 1



## 5. Control Design: Outputs

	RegDst	ALUSrc	MemToReg	RegWrite	MemRead	MemWrite	Branch	ALUop	
								op1	op0
R-type	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

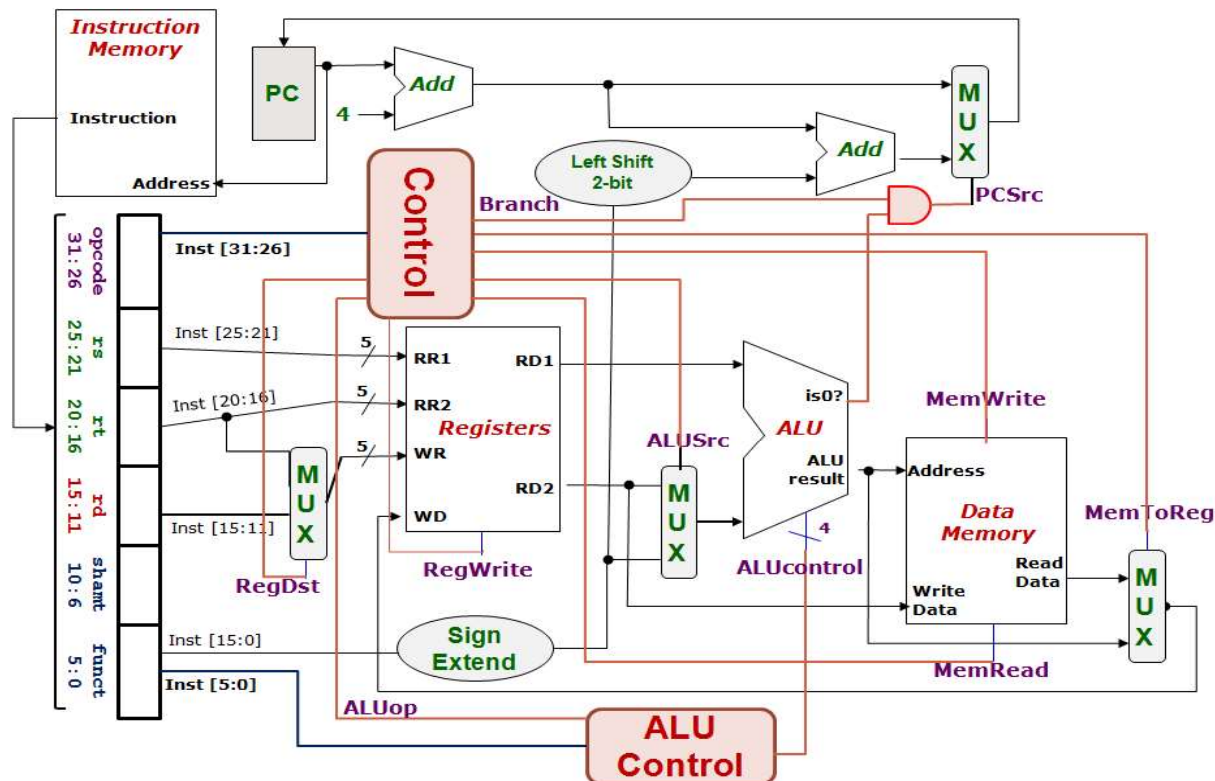


## 5. Control Design: Inputs

	Opcode ( Op[5:0] == Inst[31:26] )						
	Op5	Op4	Op3	Op2	Op1	Op0	Value in Hexadecimal
<b>R-type</b>	0	0	0	0	0	0	0
<b>lw</b>	1	0	0	0	1	1	23
<b>sw</b>	1	0	1	0	1	1	2B
<b>beq</b>	0	0	0	1	0	0	4

- With the input (opcode) and output (control signals), let's design the circuit
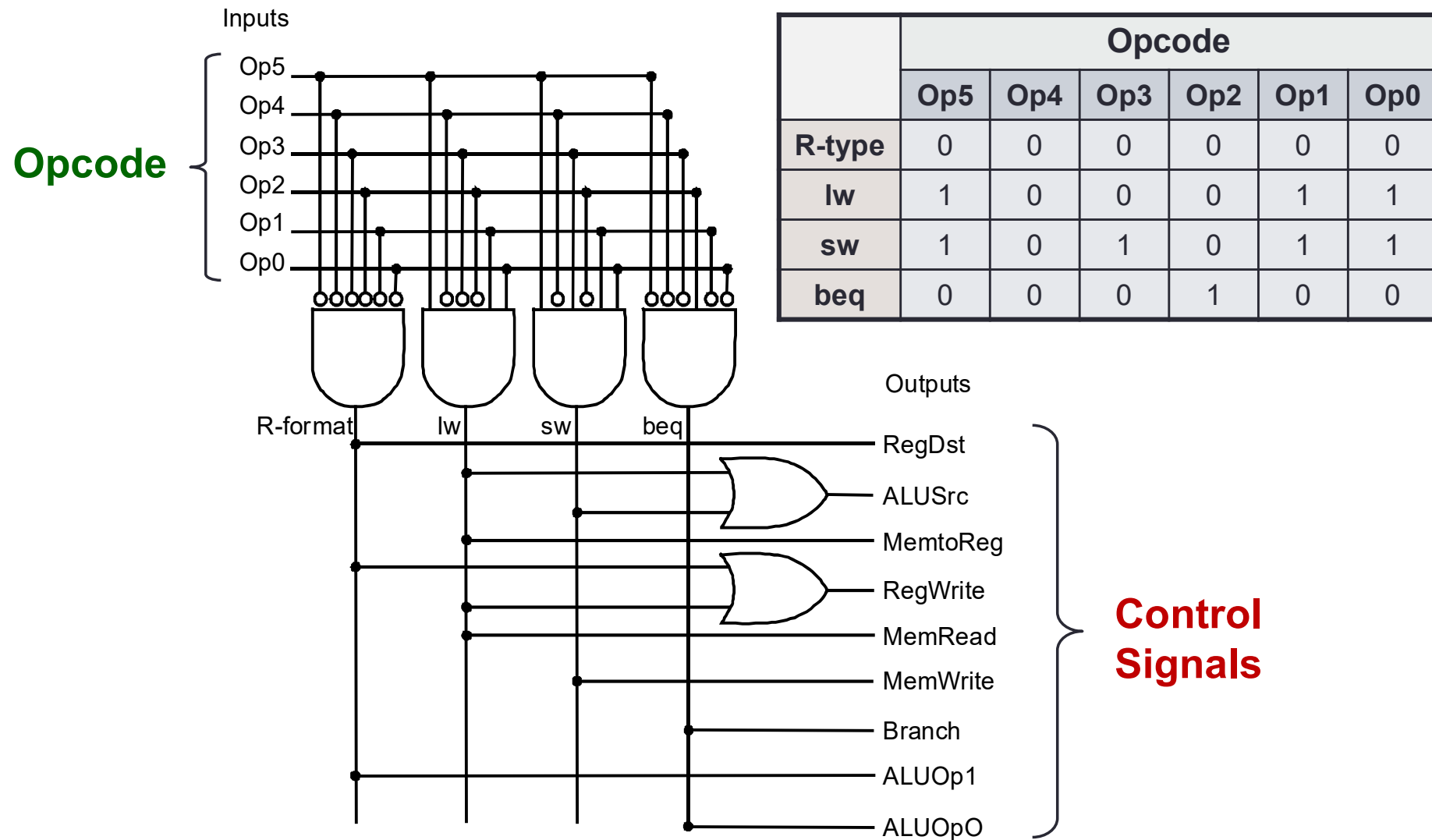
## 5. Combinational Circuit Implementation



## 5. Combinational Circuit Implementation

