

CS2100

COMPUTER ORGANISATION

<http://www.comp.nus.edu.sg/~cs2100/>

Lecture #19

Sequential Logic



NUS
National University
of Singapore

School of
Computing

Lecture #19: Sequential Logic (1/2)

1. Introduction
2. Memory Elements
3. Latches
 - 3.1 *S-R* Latch
 - 3.2 *D* Latch
4. Flip-flops
 - 4.1 *S-R* Flip-flop
 - 4.2 *D* Flip-flop
 - 4.3 *J-K* Flip-flop
 - 4.4 *T* Flip-flop

Lecture #19: Sequential Logic (2/2)


- 5. Asynchronous Inputs
- 6. Synchronous Sequential Circuit
 - 6.1 Flip-flop Characteristic Tables
 - 6.2 Analysis
 - 6.3 Flip-flop Excitation Tables
 - 6.4 Design
- 7. Memory
 - 7.1 Memory Unit
 - 7.2 Read/Write Operations
 - 7.3 Memory Cell
 - 7.4 Memory Arrays

1. Introduction (1/2)

- Two classes of logic circuits
 - Combinational
 - Sequential


- **Combinational Circuit**

 - Each output depends entirely on the immediate (present) inputs.



- **Sequential Circuit**

 - Each output depends on both present inputs and state.




1. Introduction (2/2)

- Two types of sequential circuits:
 - **Synchronous**: outputs change only at specific time
 - **Asynchronous**: outputs change at any time
- Multivibrator: a class of sequential circuits
 - Bistable (2 stable states)
 - Monostable or one-shot (1 stable state)
 - Astable (no stable state)
- Bistable logic devices
 - **Latches** and **flip-flops**.
 - They differ in the methods used for changing their state.

 2. Memory Elements (1/3)

- **Memory element**: a device which can remember value indefinitely, or change value on command from its inputs.



- **Characteristic table:**


Command (at time t)	$Q(t)$	$Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1

$Q(t)$ or Q : current state


$Q(t+1)$ or Q^+ : next state

2. Memory Elements (2/3)

- Memory element with clock.

 

- Clock** is usually a square wave.

 

2. Memory Elements (3/3)

- Two types of triggering/activation


- Pulse-triggered
- Edge-triggered

- Pulse-triggered

- Latches
- ON = 1, OFF = 0

- Edge-triggered

 - Flip-flops
- Positive edge-triggered (ON = from 0 to 1; OFF = other time)
- Negative edge-triggered (ON = from 1 to 0; OFF = other time)




3.1 ^{set reset latch} S-R Latch (1/3)

- Two inputs: S and R .
- Two complementary outputs: Q and Q' .
 - When $Q = \text{HIGH}$, we say latch is in **SET** state.
 - When $Q = \text{LOW}$, we say latch is in **RESET** state.
- For active-high input S-R latch (also known as NOR gate latch)
 - $R = \text{HIGH}$ and $S = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
 - $S = \text{HIGH}$ and $R = \text{LOW} \rightarrow Q$ becomes HIGH (SET state)
 - Both R and S are LOW \rightarrow No change in output Q
 - Both R and S are HIGH \rightarrow Outputs Q and Q' are both LOW (invalid!)
- Drawback: invalid condition exists and must be avoided.


3.1 S-R Latch (2/3)

will stabilise after 3 tricks

- Active-high input S-R latch:

 


- Block diagram:

 

 3.1 S-R Latch (3/3)

- **Characteristic table** for active-high input S - R latch:



S	R	Q	Q'	
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

S	R	$Q(t+1)$
0	0	$Q(t)$ No change
0	1	0 Reset
1	0	1 Set
1	1	indeterminate

$Q(t+1) = ?$ $\begin{matrix} S' \\ S \end{matrix}$

0	1	0	0
1	1	X	X



$\hookrightarrow = S + Q \cdot R'$

$\& S \cdot R = 0$

$\underbrace{\hspace{10em}}_Q$

  3.1 Active-Low S-R Latch

- (You may skip this slide.)
- What we have seen is **active-high input S-R** latch.
- There are **active-low input S-R** latches, where NAND gates are used instead. See diagram on the left below.




- In this case,
 - when $R=0$ and $S=1$, the latch is reset (i.e. Q becomes 0)
 - when $R=1$ and $S=0$, the latch is set (i.e. Q becomes 1)
 - when $S=R=1$, it is a no-change command.
 - when $S=R=0$, it is an invalid command.
- Sometimes, we use the alternative gate diagram for the NAND gate. See diagram on the right above. (This appears in more complex latches/flip-flops in the later slides.)

(Sometimes, the inputs are labelled as S' and R' .)

S	R	A-Hi	A-Low
1	0	Set	Reset
0	1	Reset	Set
0	0	NC	X
1	1	X	NC

 3.1 Gated S-R Latch

- S-R latch + *enable input* (EN) and 2 NAND gates → a **gated S-R latch**.




- Outputs change (if necessary) only when EN is high.

If enable = 0; then it is automatically a nochange command

 3.2 Gated D Latch (1/2)

- Make input R equal to S' \rightarrow gated D latch.
- D latch eliminates the undesirable condition of invalid state in the S - R latch.



$D = 0$, Reset command

$D = 1$, Set command

$E = 0$, No change command

3.2 Gated D Latch (2/2)


- When EN is high,
 - $D = \text{HIGH} \rightarrow$ latch is SET
 - $D = \text{LOW} \rightarrow$ latch is RESET
- Hence when EN is high, Q “follows” the D (data) input.
- **Characteristic table:**

EN	D	$Q(t+1)$	
1	0	0	Reset
1	1	1	Set
0	X	$Q(t)$	No change

When $EN=1$, $Q(t+1) = ? D$

 
4. Flip-flops (1/2)

- Flip-flops are synchronous bistable devices.
- Output changes state at a specified point on a triggering input called the **clock**.
- Change state either at the positive (rising) edge, or at the negative (falling) edge of the clock signal.




 4. Flip-flops (2/2)

- *S-R* flip-flop, *D* flip-flop, and *J-K* flip-flop.
- Note the “>” symbol at the clock input.




Positive edge-triggered flip-flops

 

Negative edge-triggered flip-flops

 4.1 S-R Flip-flop

- **S-R flip-flop**: On the triggering edge of the clock pulse,
 - $R = \text{HIGH}$ and $S = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
 - $S = \text{HIGH}$ and $R = \text{LOW} \rightarrow Q$ becomes HIGH (SET state)
 - Both R and S are LOW \rightarrow No change in output Q
 - Both R and S are HIGH \rightarrow Invalid!
- **Characteristic table** of positive edge-triggered S-R flip-flop:




S	R	CLK	$Q(t+1)$	Comments
0	0	X	$Q(t)$	No change
0	1	\uparrow	0	Reset
1	0	\uparrow	1	Set
1	1	\uparrow	?	Invalid

X = irrelevant ("don't care")

\uparrow = clock transition LOW to HIGH

 4.2 D Flip-flop (1/2)

- **D flip-flop**: Single input D (data). On the triggering edge of the clock pulse,
 - $D = \text{HIGH} \rightarrow Q$ becomes HIGH (SET state)
 - $D = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
- Hence, Q “follows” D at the clock edge.
- Convert S-R flip-flop into a D flip-flop: add an inverter.




A positive edge-triggered D flip-flop formed with an S-R flip-flop.

D	CLK	$Q(t+1)$	Comments
1	↑	1	Set
0	↑	0	Reset

↑ = clock transition LOW to HIGH

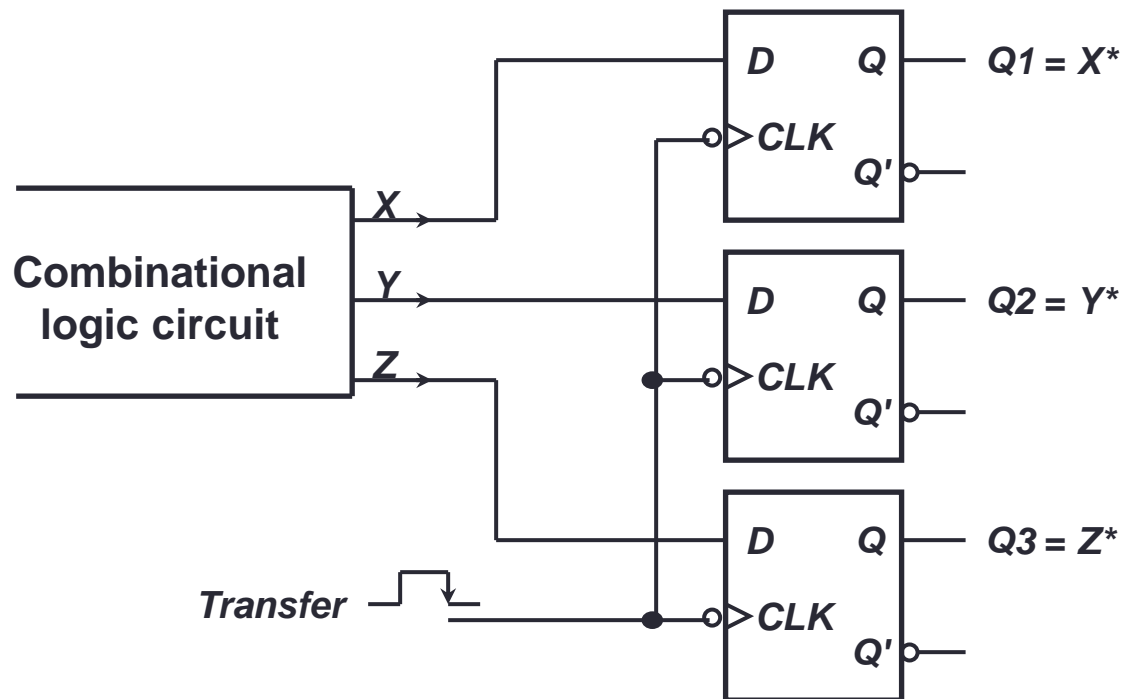4.2 D Flip-flop (2/2)

- Application: Parallel data transfer.
 - To transfer logic-circuit outputs X , Y , Z to flip-flops $Q1$, $Q2$ and $Q3$ for storage.




* After occurrence of negative-going transition

4.3 *J-K* Flip-flop (1/2)

- *J-K* flip-flop: Q and Q' are fed back to the pulse-steering NAND gates.
- No invalid state.
- Include a toggle state
 - $J = \text{HIGH}$ and $K = \text{LOW} \rightarrow Q$ becomes HIGH (SET state)
 - $K = \text{HIGH}$ and $J = \text{LOW} \rightarrow Q$ becomes LOW (RESET state)
 - Both J and K are LOW \rightarrow No change in output Q
 - Both J and K are HIGH \rightarrow Toggle

4.3 J-K Flip-flop (2/2)

- J-K flip-flop circuit:

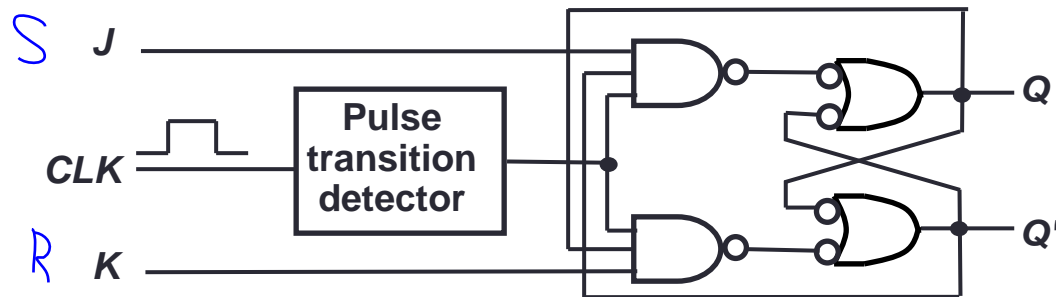

- Characteristic table:


J	K	CLK	$Q(t+1)$	Comments
0	0	↑	$Q(t)$	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	$Q(t)'$	Toggle

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$Q(t+1) = ? J \cdot Q' + K' \cdot Q$$

 4.4 T Flip-flop

- T flip-flop: Single input version of the J - K flip-flop, formed by tying both inputs together.



- Characteristic table:

T	CLK	$Q(t+1)$	Comments
0	↑	$Q(t)$	No change
1	↑	$Q(t)'$	Toggle

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = ? \quad T \cdot Q' + T' \cdot Q$$

5. Asynchronous Inputs (1/2)


- S - R , D and J - K inputs are **synchronous inputs**, as data on these inputs are transferred to the flip-flop's output only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock; example: *preset* (PRE) and *clear* (CLR) [or *direct set* (SD) and *direct reset* (RD)].
- When $PRE=HIGH$, Q is immediately set to HIGH.
- When $CLR=HIGH$, Q is immediately cleared to LOW.
- Flip-flop in normal operation mode when both PRE and CLR are LOW.



useful to set Q all to 1/0 at the start of the experiment

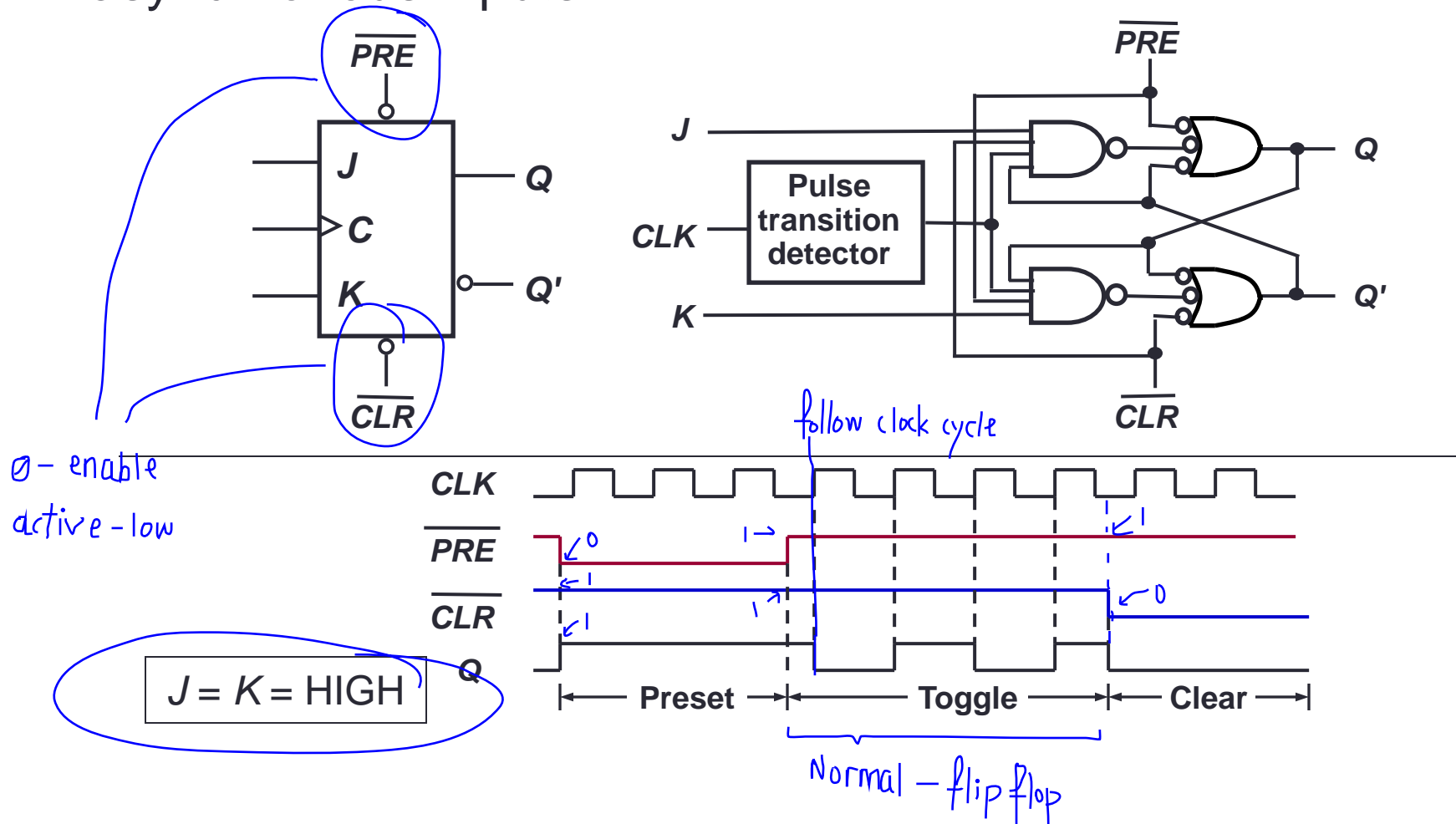5. Asynchronous Inputs (2/2)

- A J - K flip-flop with active-low PRESET and CLEAR asynchronous inputs.



6. Synchronous Sequential Circuits

- Building blocks: logic gates and flip-flops.
- Flip-flops make up the memory while the gates form one or more combinational sub-circuits.
- We have discussed S - R flip-flop, J - K flip-flop, D flip-flop and T flip-flop.

6.1 Flip-flop Characteristic Tables

- Each type of flip-flop has its own behaviour, shown by its **characteristic table**.

J	K	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)'$	Toggle

S	R	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Unpredictable

D	$Q(t+1)$
0	0 Reset
1	1 Set

T	$Q(t+1)$
0	$Q(t)$ No change
1	$Q(t)'$ Toggle

6.2 Sequential Circuits: Analysis (1/7)

- Given a sequential circuit diagram, we can analyze its behaviour by deriving its *state table* and hence its *state diagram*.
- Requires *state equations* to be derived for the flip-flop inputs, as well as *output functions* for the circuit outputs other than the flip-flops (if any).
- We use $\mathbf{A}(t)$ and $\mathbf{A}(t+1)$ (or simply \mathbf{A} and \mathbf{A}^+) to represent the present state and next state, respectively, of a flip-flop represented by A .

6.2 Sequential Circuits: Analysis (2/7)

■ Example using *D* flip-flops

State equations:

$$A^+ = A \cdot x + B \cdot x$$

$$B^+ = A' \cdot x$$

Output function:

$$y = (A + B) \cdot x'$$

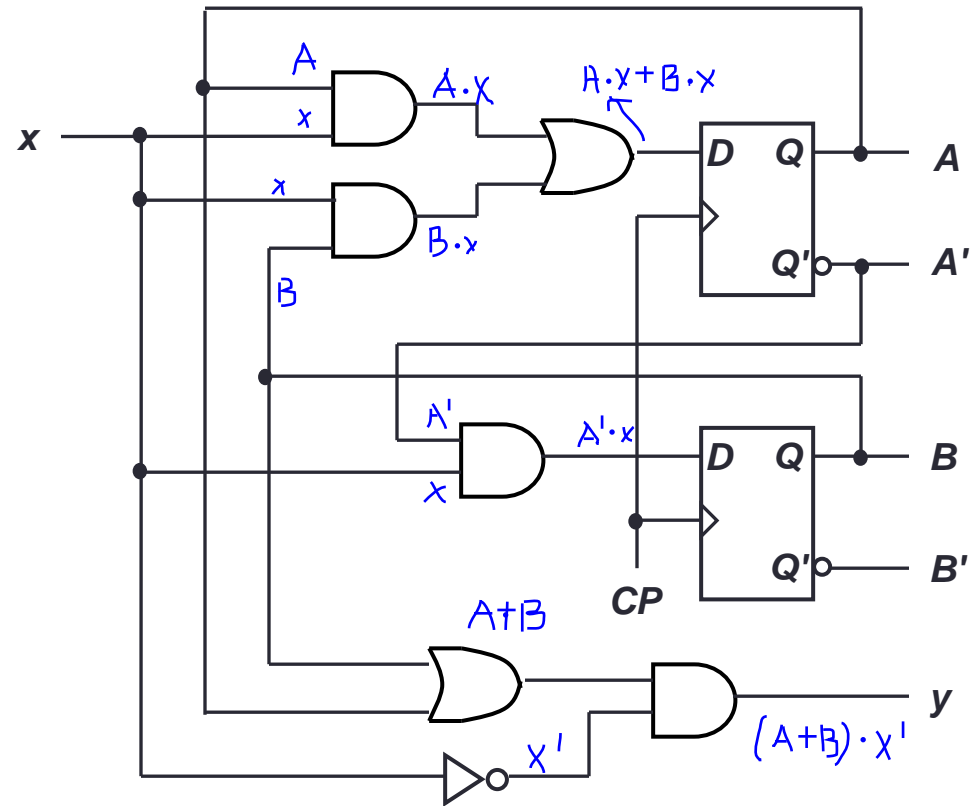


Figure 1

6.2 Sequential Circuits: Analysis (3/7)

- From the *state equations* and *output function*, we derive the **state table**, consisting of all possible binary combinations of present states and inputs.
- State table
 - Similar to truth table.
 - Inputs and present state on the left side.
 - Outputs and next state on the right side.
- m flip-flops and n inputs $\rightarrow 2^{m+n}$ rows.

6.2 Sequential Circuits: Analysis (4/7)

- **State table** for circuit of Figure 1:

State equations:

$$A^+ = A \cdot x + B \cdot x$$

$$B^+ = A' \cdot x$$

Output function:

$$y = (A + B) \cdot x'$$

Present State		Input	Next State		Output
A	B		A ⁺	B ⁺	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

6.2 Sequential Circuits: Analysis (5/7)

- Alternative form of state table:

Full table

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i> ⁺	<i>B</i> ⁺	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Compact table

Present State	Next State		Output	
	<i>x</i> =0	<i>x</i> =1	<i>x</i> =0	<i>x</i> =1
<i>AB</i>	<i>A</i> ⁺ <i>B</i> ⁺	<i>A</i> ⁺ <i>B</i> ⁺	<i>y</i>	<i>y</i>
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

6.2 Sequential Circuits: Analysis (6/7)


- From the *state table*, we can draw the *state diagram*.
- State diagram
 - Each state is denoted by a circle.
 - Each arrow (between two circles) denotes a transition of the sequential circuit (a row in state table).
 - A label of the form a/b is attached to each arrow where a (if there is one) denotes the inputs while b (if there is one) denotes the outputs of the circuit in that transition.
- Each combination of the flip-flop values represents a state. Hence, m flip-flops \rightarrow up to 2^m states.

6.2 Sequential Circuits: Analysis (7/7)

- **State diagram** of the circuit of Figure 1:

Present State	Next State		Output	
	$x=0$	$x=1$	$x=0$	$x=1$
AB	A^+B^+	A^+B^+	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

DONE!

 

6.2 Flip-flop Input Functions (1/3)


- The outputs of a sequential circuit are functions of the present states of the flip-flops and the inputs. These are described algebraically by the *circuit output functions*.
 - In Figure 1: $y = (A + B) \cdot x'$
- The part of the circuit that generates inputs to the flip-flops are described algebraically by the *flip-flop input functions* (or *flip-flop input equations*).
- The flip-flop input functions determine the next state generation.
- From the flip-flop input functions and the characteristic tables of the flip-flops, we obtain the next states of the flip-flops.

6.2 Flip-flop Input Functions (2/3)

- Example: circuit with a JK flip-flop.
- We use 2 letters to denote each flip-flop input: the first letter denotes the input of the flip-flop (J or K for J - K flip-flop, S or R for S - R flip-flop, D for D flip-flop, T for T flip-flop) and the second letter denotes the name of the flip-flop.

$$JA = B \cdot C' \cdot x + B' \cdot C \cdot x'$$

$$KA = B + y$$

 

6.2 Flip-flop Input Functions (3/3)

- In Figure 1, we obtain the following **state equations** by observing that $Q^+ = DQ$ for a D flip-flop:

$$A^+ = A \cdot x + B \cdot x \quad (\text{since } DA = A \cdot x + B \cdot x)$$

$$B^+ = A' \cdot x \quad (\text{since } DB = A' \cdot x)$$


 


Figure 1

 6.2 Analysis: Example #2 (1/3)

- Given Figure 2, a sequential circuit with two J - K flip-flops A and B , and one input x .



- Obtain the **flip-flop input functions** from the circuit:

$$JA = B$$

$$JB = x'$$

$$KA = B \cdot x'$$

$$KB = A' \cdot x + A \cdot x' = A \oplus x$$

6.2 Analysis: Example #2 (2/3)

$$JA = B$$

$$KA = B \cdot x'$$

$$JB = x'$$

$$KB = A' \cdot x + A \cdot x' = A \oplus x$$

- Fill the **state table** using the above functions, knowing the characteristics of the flip-flops used.


<i>J</i>	<i>K</i>	<i>Q(t+1)</i>	Comments
0	0	<i>Q(t)</i>	No change
0	1	0	Reset
1	0	1	Set
1	1	<i>Q(t)'</i>	Toggle

Present state		Input <i>x</i>	Next state		Commands			
<i>A</i>	<i>B</i>		<i>A</i> ⁺	<i>B</i> ⁺	<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

6.2 Analysis: Example #2 (3/3)


- Draw the **state diagram** from the state table.

Present state		Input x	Next state		Flip-flop inputs			
A	B		A^+	B^+	J_A	K_A	J_B	K_B
0	0	0			0	0	1	0
0	0	1			0	0	0	1
0	1	0			1	1	1	0
0	1	1			1	0	0	1
1	0	0			0	0	1	1
1	0	1			0	0	0	0
1	1	0			1	1	1	1
1	1	1			1	0	0	0

 

 6.2 Analysis: Example #3 (1/3)

- Derive the state table and state diagram of this circuit.



- Flip-flop input functions:

$$JA = B$$

$$KA = B'$$

$$JB = KB = (A \oplus x)' = A \cdot x + A' \cdot x'$$

6.2 Analysis: Example #3 (2/3)

- Flip-flop input functions:

$$JA = B$$

$$KA = B'$$

$$JB = KB = (A \oplus x)' = A \cdot x + A' \cdot x'$$

$$y = B \oplus (A \oplus x)$$

- State table:


fill this first

Present state		Input x	Next state		Output y	Flip-flop inputs			
A	B		A^+	B^+		JA	KA	JB	KB
0	0	0	0	1	0	0	1	1	1
0	0	1	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	1	1
0	1	1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	1	0	0
1	0	1	0	1	0	0	1	1	1
1	1	0	1	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1	1

6.2 Analysis: Example #3 (3/3)

■ State diagram:

Present state		Input x	Next state		Output y	Flip-flop inputs			
A	B		A^+	B^+		J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	1	1
0	0	1	0	0	1	0	1	0	0
0	1	0	1	0	1	1	0	1	1
0	1	1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	1	0	0
1	0	1	0	1	0	0	1	1	1
1	1	0	1	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1	1

 

6.3 Flip-flop Excitation Tables (1/2)

- *Analysis*: Starting from a circuit diagram, derive the state table or state diagram.
- *Design*: Starting from a set of specifications (in the form of state equations, state table, or state diagram), derive the logic circuit.
- *Characteristic tables* are used in analysis.
- *Excitation tables* are used in design.

6.3 Flip-flop Excitation Tables (1/2)

- **Excitation tables:** given the required transition from present state to next state, determine the flip-flop input(s).

Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop

Q	Q^+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR Flip-flop

Q	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-flop

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0

T Flip-flop


working backwards, with Q and Q^+ , we know what the command was

6.4 Sequential Circuits: Design

- Design procedure:
 - Start with circuit specifications – description of circuit behaviour, usually a state diagram or state table.
 - Derive the state table.
 - Perform state reduction if necessary.
 - Perform state assignment.
 - Determine number of flip-flops and label them.
 - Choose the type of flip-flop to be used.
 - Derive circuit excitation and output tables from the state table.
 - Derive circuit output functions and flip-flop input functions.
 - Draw the logic diagram.

 6.4 Design: Example #1 (1/5)

- Given the following state diagram, design the sequential circuit using *JK* flip-flops.



Questions:

How many flip-flops are needed?

How many input variable are there?

1) see how many states


1.1) determine number of flipflops

2) see how many inputs and outputs

2.1) give them names

 6.4 Design: Example #1 (2/5)

- Circuit state/excitation table, using JK flip-flops.



Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


JK Flip-flop's
excitation table.

Present State	Next State	
	$x=0$	$x=1$
AB	A^+B^+	A^+B^+
00	00	01
01	10	01
10	10	11
11	11	00

Present state		Input	Next state		Flip-flop inputs			
A	B		A^+	B^+	JA	KA	JB	KB
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

6.4 Design: Example #1 (3/5)

- Block diagram.

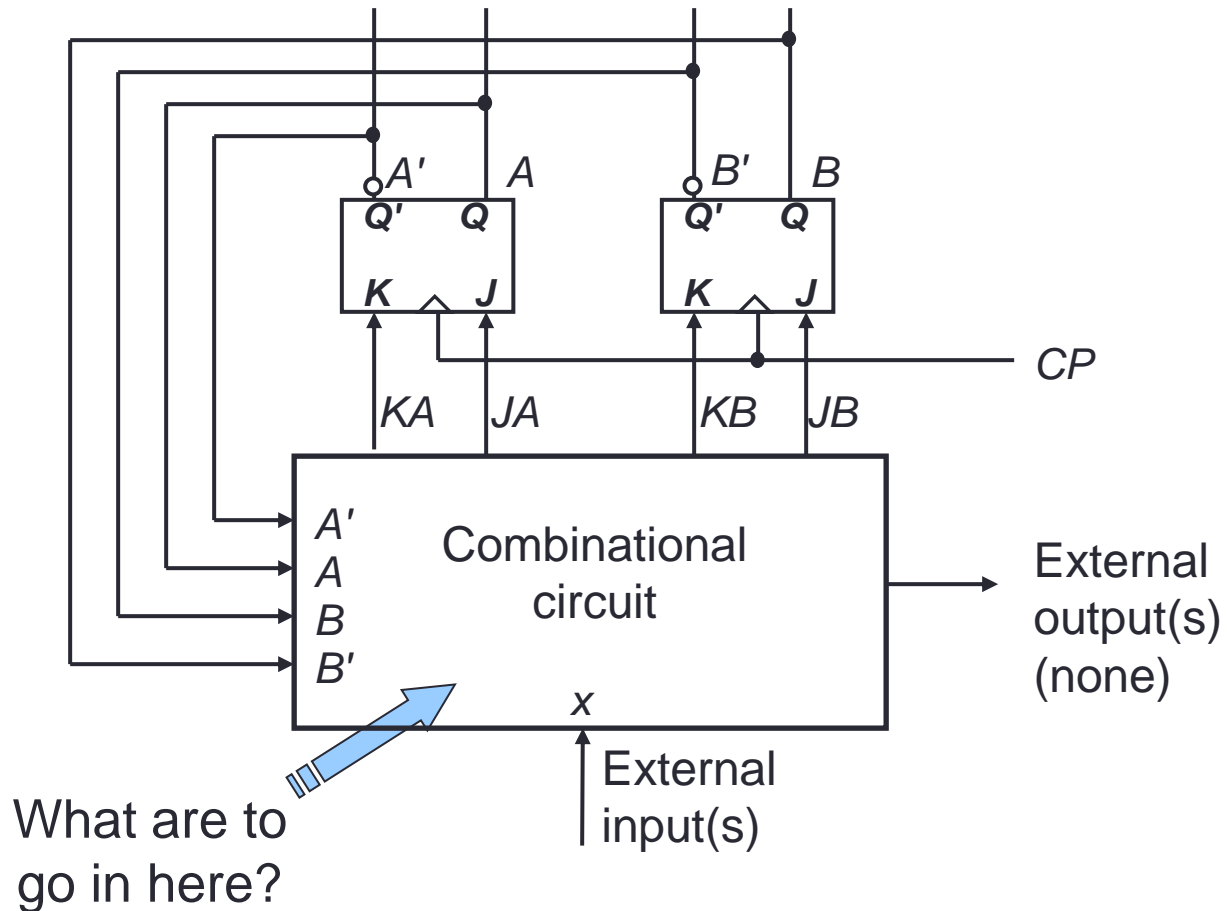

6.4 Design: Example #1 (4/5)

- From **state table**, get **flip-flop input functions**.

Present state		Input x	Next state		Flip-flop inputs			
A	B		A^+	B^+	JA	KA	JB	KB
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Bx

 $A \backslash$

	00	01	11	10
0		1	X	X
1		1	X	X

 x

 $JB = x$

Bx

 $A \backslash$

	00	01	11	10
0	X	X		1
1	X	X	1	

 x

 $KB = (A \oplus x)'$

Bx

 $A \backslash$

	00	01	11	10
0				1
1	X	X	X	X

 x

 $JA = B \cdot x'$

Bx

 $A \backslash$

	00	01	11	10
0	X	X	X	X
1			1	

 x

 $KA = B \cdot x$

6.4 Design: Example #1 (5/5)

- Flip-flop input functions:


$$JA = B \cdot x'$$

$$JB = x$$

$$KA = B \cdot x$$

$$KB = (A \oplus x)'$$

- Logic diagram:

 

6.4 Design: Example #2 (1/3)

- Using D flip-flops, design the circuit based on the state table below. (Exercise: Design it using JK flip-flops.)

Present state		Input	Next state		Output
A	B		A^+	B^+	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

6.4 Design: Example #2 (2/3)

- Determine expressions for flip-flop inputs and the circuit output y . $Q^+ = D$

Present state		Input x	Next state		Output y
A	B		A^+	B^+	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

$$DA(A,B,x) = \sum m(2,4,5,6)$$

$$DB(A,B,x) = \sum m(1,3,5,6)$$

$$y(A,B,x) = \sum m(1,5)$$

		Bx			
		00	01	11	10
A	0				1
	1	1	1		1

$$DA = A \cdot B' + B \cdot x'$$

		Bx			
		00	01	11	10
A	0		1	1	
	1		1		1

$$DB = A' \cdot x + B' \cdot x' + A \cdot B \cdot x'$$

		Bx			
		00	01	11	10
A	0		1		
	1		1		

$$y = B' \cdot x$$


6.4 Design: Example #2 (3/3)

- From derived expressions, draw logic diagram:

$$DA = A \cdot B' + B \cdot x'$$

$$DB = A' \cdot x + B' \cdot x + A \cdot B \cdot x'$$

$$y = B' \cdot x$$

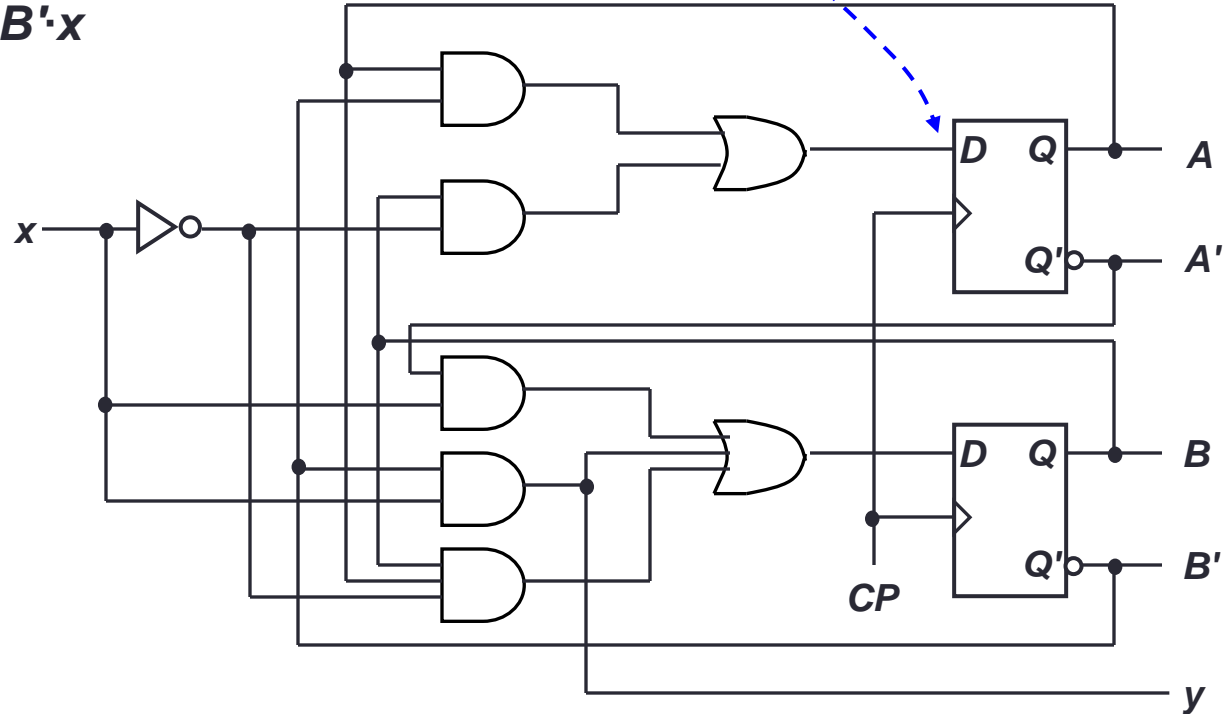

6.4 Design: Example #3 (1/4)

When the states are not of power 2

- Design involving unused states.

2 FFs
5 States

Present state			Input	Next state			Flip-flop inputs						Output
A	B	C		A ⁺	B ⁺	C ⁺	SA	RA	SB	RB	SC	RC	
0	0	1	0	0	0	1	0	X	0	X	X	0	0
0	0	1	1	0	1	0	0	X	1	0	0	1	0
0	1	0	0	0	1	1	0	X	X	0	1	0	0
0	1	0	1	1	0	0	1	0	0	1	0	X	0
0	1	1	0	0	0	1	0	X	0	1	X	0	0
0	1	1	1	1	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	1	X	0	0	X	1	0	0
1	0	0	1	1	0	0	X	0	0	X	0	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0
1	0	1	1	1	0	0	X	0	0	X	0	1	1

Given these

Derive these

Are there other unused states?

Unused state 000:

0	0	0	0	X	X	X	X	X	X	X	X	X	X
0	0	0	1	X	X	X	X	X	X	X	X	X	X

110

111

6.4 Design: Example #3 (2/4)

- From state table, obtain expressions for flip-flop inputs.

SA = ?

$AB \backslash Cx$		C			
		00	01	11	10
A	00	X	X		
	01		1	1	
	11	X	X	X	X
	10	X	X	X	

x

B

RA = ?

$AB \backslash Cx$		C			
		00	01	11	10
A	00	X	X	X	X
	01	X			X
	11	X	X	X	X
	10				1

x

B

SB = ?

$AB \backslash Cx$		C			
		00	01	11	10
A	00	X	X	1	
	01	X			
	11	X	X	X	X
	10				

x

B

RB = ?

$AB \backslash Cx$		C			
		00	01	11	10
A	00	X	X		X
	01		1	1	1
	11	X	X	X	X
	10	X	X	X	X

x

B

6.4 Design: Example #3 (3/4)

- From state table, obtain expressions for flip-flop inputs (cont'd).

$SC = ?$

$AB \backslash Cx$		C			
		00	01	11	10
A	00	X	X		X
	01	1			X
	11	X	X	X	X
	10	1			X

x

$RC = ?$

$AB \backslash Cx$		C			
		00	01	11	10
A	00	X	X	1	
	01		X	1	
	11	X	X	X	X
	10		X	1	

x

$AB \backslash Cx$		C			
		00	01	11	10
A	00	X	X		
	01				
	11	X	X	X	X
	10		1	1	

x

$y = ?$

6.4 Design: Example #3 (4/4)

- From derived expressions, draw the logic diagram:

$$SA = B \cdot x$$

$$RA = C \cdot x'$$


$$SB = A' \cdot B' \cdot x$$

$$RB = B \cdot C + B \cdot x$$

$$SC = x'$$

$$RC = x$$

$$y = A \cdot x$$

 


7. Memory (1/4)

- Memory stores programs and data.
- Definitions:
 - 1 byte = 8 bits
 - 1 word: in multiple of bytes, a unit of transfer between main memory and registers, usually size of register.
 - 1 KB (kilo-bytes) = 2^{10} bytes; 1 MB (mega-bytes) = 2^{20} bytes; 1 GB (giga-bytes) = 2^{30} bytes; 1 TB (tera-bytes) = 2^{40} bytes.
- **Desirable properties:** fast access, large capacity, economical cost, non-volatile.
- However, most memory devices do not possess all these properties.

7. Memory (2/4)

Memory hierarchy

 


Fast, expensive
(small numbers),
volatile



Slow, cheap
(large numbers),
non-volatile

7. Memory (3/4)

Data transfer

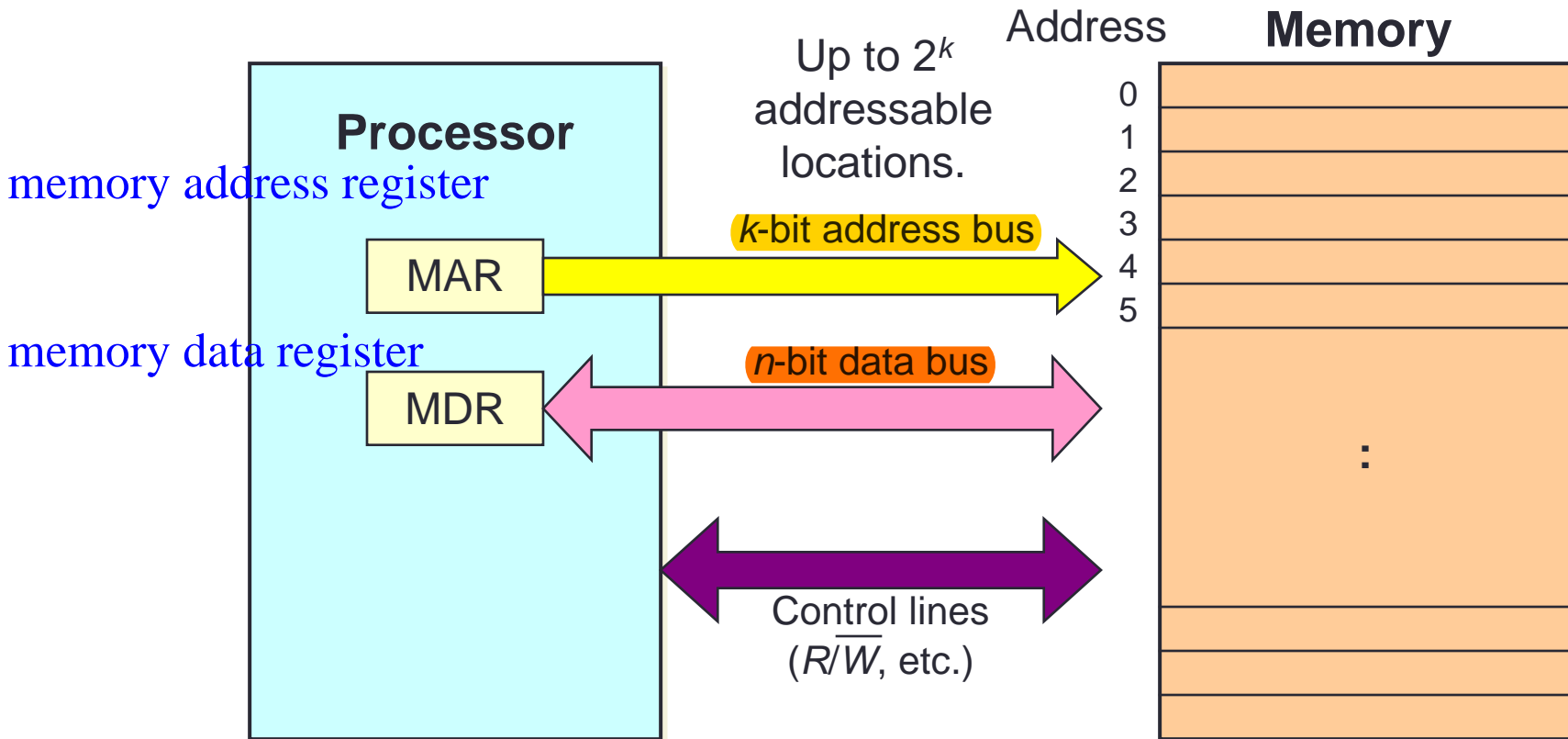


7. Memory (4/4)

- A memory unit stores binary information in groups of bits called *words*.
- The data consists of n lines (for n -bit words). **Data input lines** provide the information to be stored (*written*) into the memory, while **data output lines** carry the information out (*read*) from the memory.
- The **address** consists of k lines which specify which word (among the 2^k words available) to be selected for reading or writing.
- The control lines *Read* and *Write* (usually combined into a single control line *Read/Write*) specifies the direction of transfer of the data.

7.1 Memory Unit

- Block diagram of a memory unit:

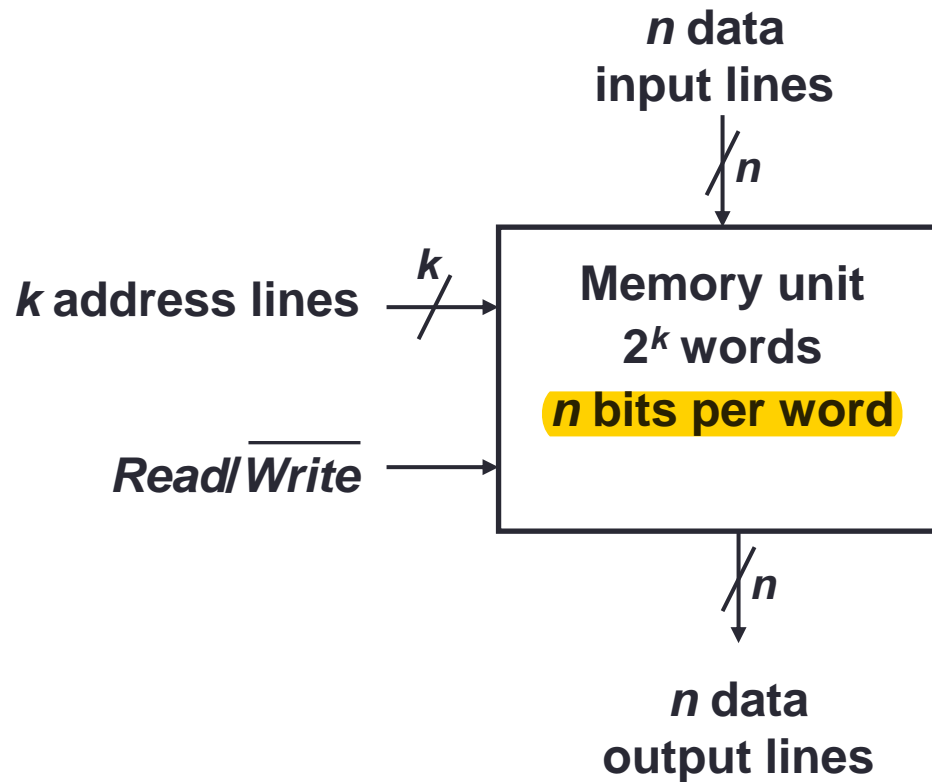


7.2 Read/Write Operations

- **Write** operation:
 - Transfers the address of the desired word to the address lines.
 - Transfers the data bits (the word) to be stored in memory to the data input lines.
 - Activates the *Write* control line (set *Read/Write* to 0).
- **Read** operation:
 - Transfers the address of the desired word to the address lines.
 - Activates the *Read* control line (set *Read/Write* to 1).


Memory Enable	<i>Read/Write</i>	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

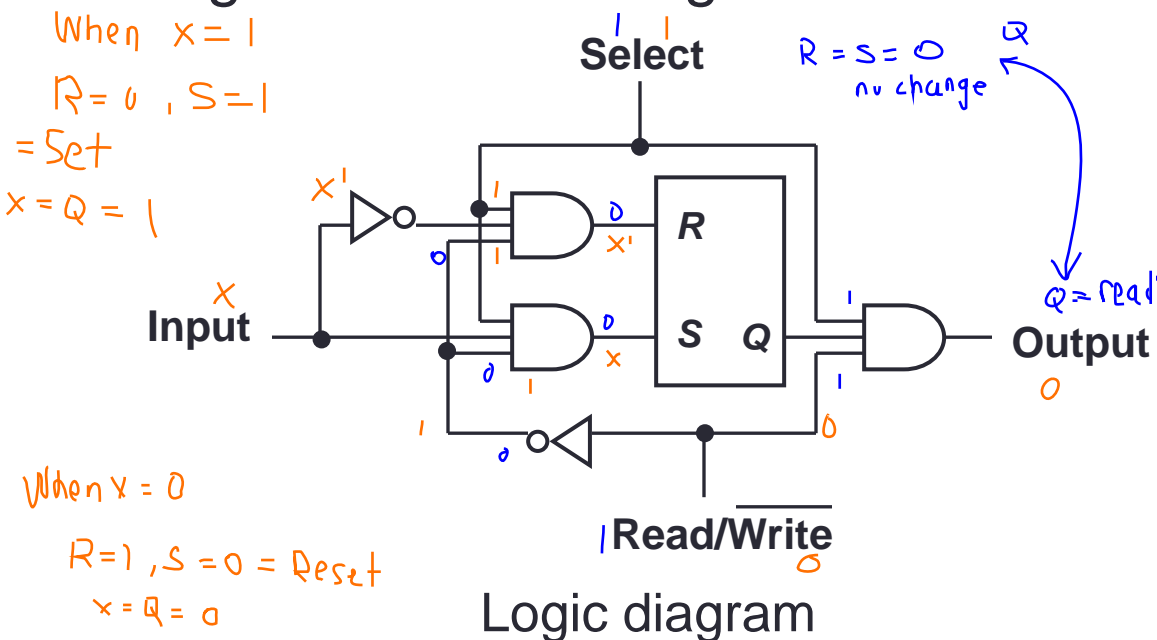7.3 Memory Cell

- Two types of RAM
 - Static RAMs use flip-flops as the memory cells.
 - Dynamic RAMs use capacitor charges to represent data. Though simpler in circuitry, they have to be constantly refreshed.
- A single memory cell of the static RAM has the following logic and block diagrams:




Binary Cell = 1 bit of data

 

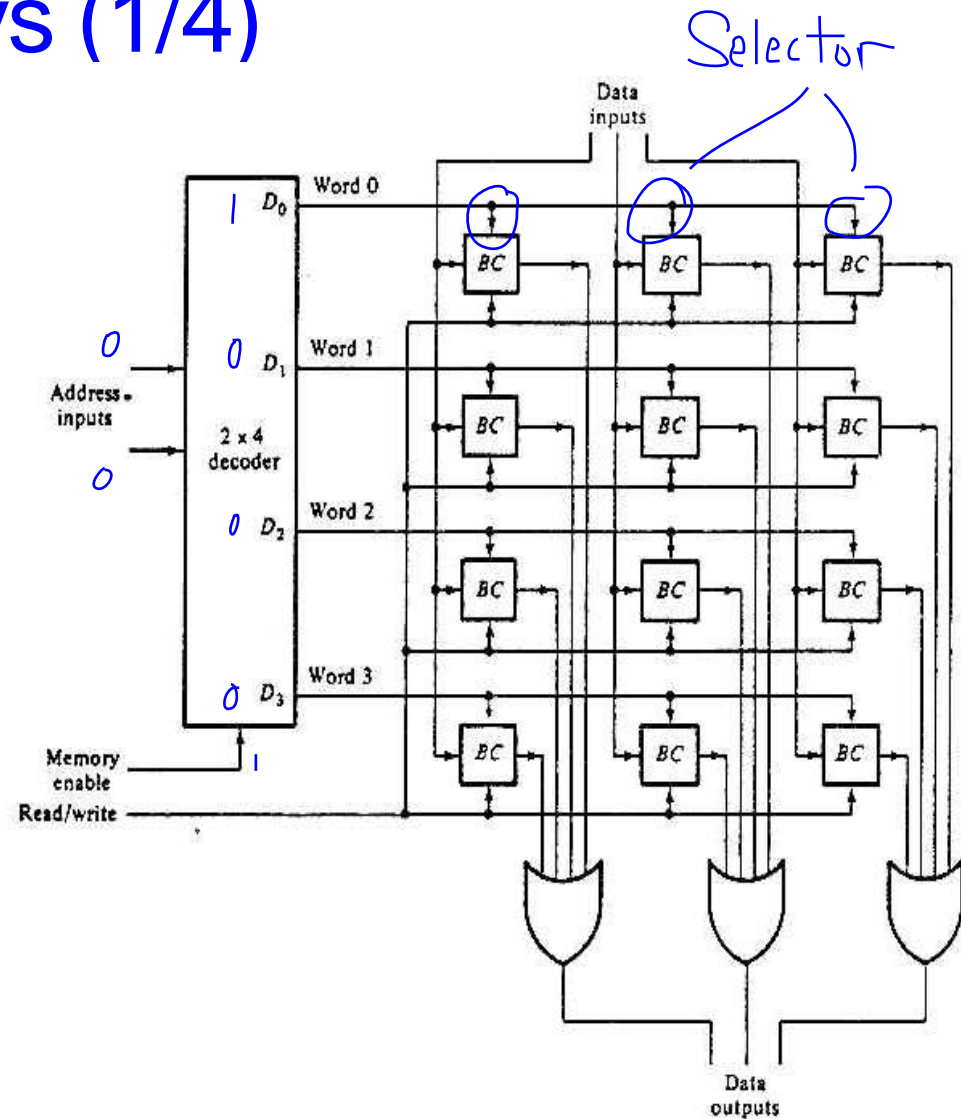
7.4 Memory Arrays (1/4)

- Logic construction of a **4×3 RAM** (with decoder and OR gates):



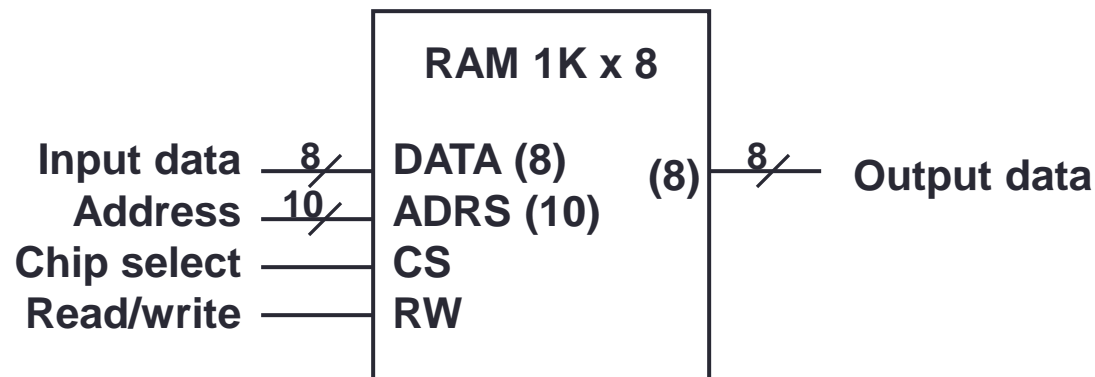
7.4 Memory Arrays (2/4)

- An array of RAM chips: memory chips are combined to form larger memory.
- A **1K × 8-bit RAM chip**:





Block diagram of a 1K x 8 RAM chip

7.4 Memory Arrays (3/4)

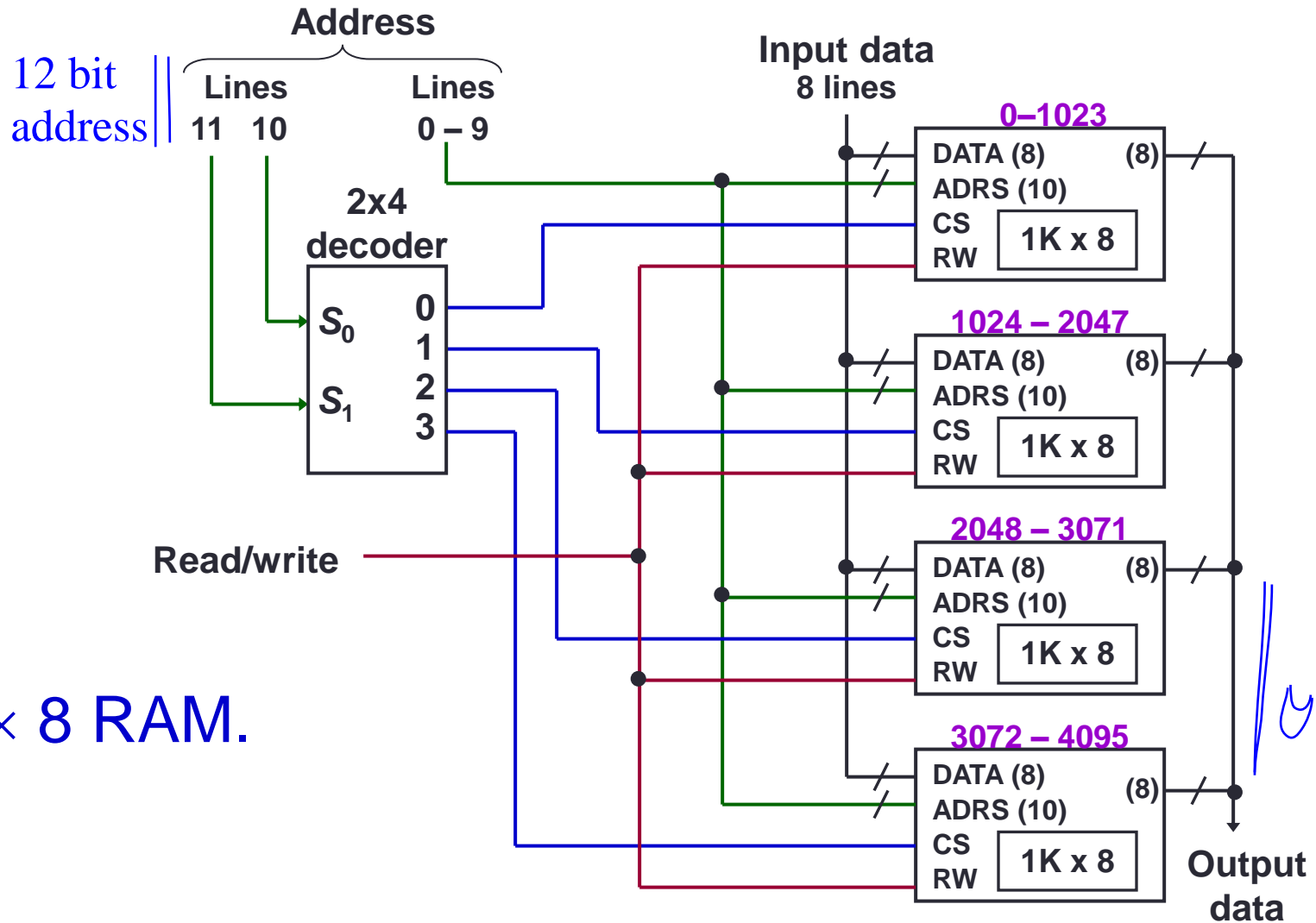

- 4K × 8 RAM.

7.4 Memory Arrays (4/4)

 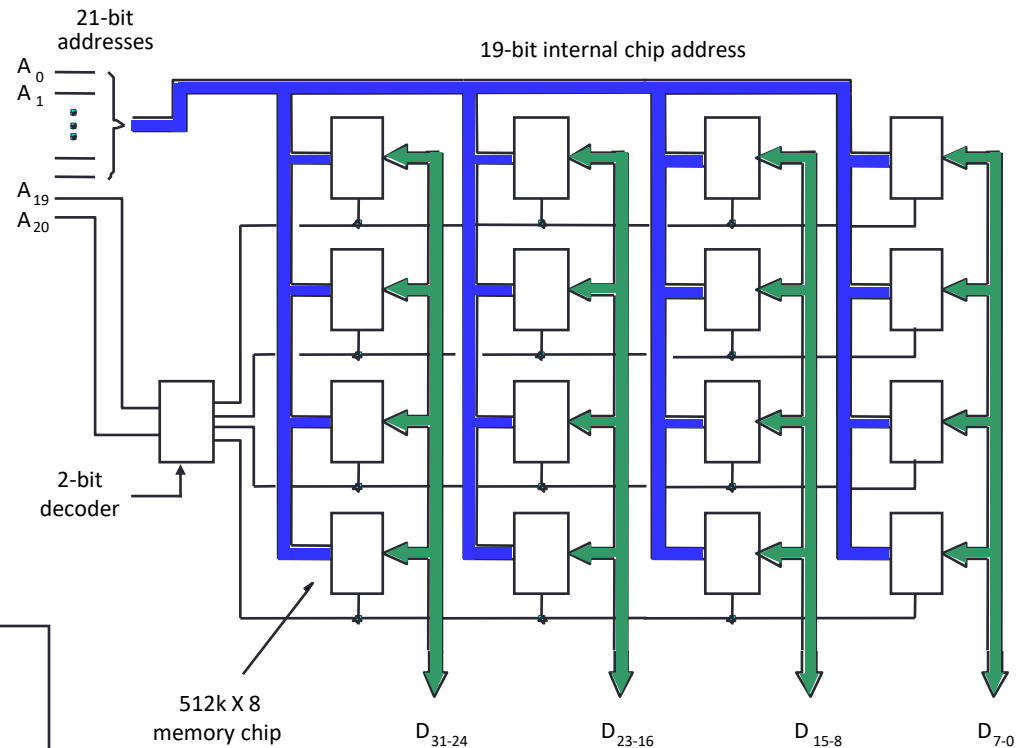

- **2M × 32** memory module
 - Using 512K × 8 memory chips.

End of File