

CS2100 (AY2020/21 Semester 2)
Assignment #3

PLEASE READ THE FOLLOWING INSTRUCTIONS VERY CAREFULLY.

1. The **deadline** for this assignment is **9 April 2021, Friday, 1pm**. The submission folders will close shortly after 1pm. Late submission will not be accepted -- you will receive 0 mark.
2. Complete this assignment **on your own** without collaborating or discussing with anyone. If found to have cheated in this assignment, you will receive an F grade for this module as well as face other disciplinary sanctions. Take this warning seriously.
3. Please submit only **ONE pdf file** called **AxxxxxxxY.pdf**, where **AxxxxxxxY** is your student number. Marks will be deducted if you deposit multiple files in the submission folder or your submitted file is not a pdf file.
4. Please keep your submission **short**. You only need to submit your answers; you do not need to include the questions.
5. Answers may be typed or handwritten. In case of the latter, please ensure that you use **dark ink** and your handwriting is **neat and legible**. Marks may be deducted for untidy work or illegible handwriting.
6. Upload your file to LumiNUS > Files > Assignment 2 > (your tutorial group) > (your personal folder).
7. There are FOUR (4) questions on SIX (6) printed pages in this paper.
8. The questions are worth **40 marks** in total.
9. **You do not need to show your working in this assignment.**

=== END OF INSTRUCTIONS ===

Question 0. Submission instructions (3 marks)


- (a) You have named your file with your student number, i.e., **AxxxxxxxY.pdf**. (1 mark)
- (b) You have submitted your assignment as a **single PDF file** and no multiple copies. (1 mark)
- (c) Your assignment submission has your **tutorial group number, student number** and **name** at the top of the first page of your file. (All three items must be present.) (1 mark)

Question 1. MSI Devices (16 marks)

Note:

- Boolean constants (0 and 1) are always available;
- Complemented literals are not available.

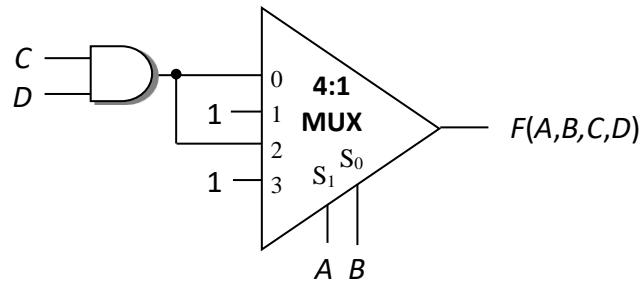- (a) Given the following circuit showing a 4:1 multiplexer and an AND gate, what is the simplified SOP expression of the function $F(A,B,C,D)$? [3 marks]



Answer: $F = B + C \cdot D$

Working: $A' \cdot B' \cdot (C \cdot D) + A' \cdot B \cdot (1) + A \cdot B' \cdot (C \cdot D) + A \cdot B \cdot (1) = B + B' \cdot C \cdot D = B + C \cdot D$

- (b) Implement the following Boolean function using a single 4:1 multiplexer without any logic gate. Once you have chosen the 2 variables for the selector lines, those 2 variables are not to appear in the 4 multiplexer inputs.


No mark will be awarded if any logic gate besides the multiplexer is used.

$$H(A,B,C,D) = \sum m(2, 7, 10, 12, 14, 15)$$

The block diagram of a 4:1 multiplexer is given in part (a) above.

[4 marks]

Answer:

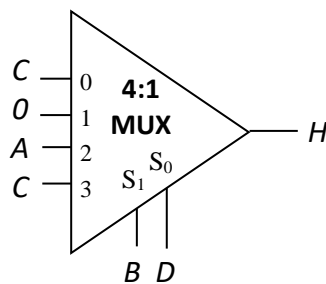

A	B	C	D	H
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1


A	B	C	D	H
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

- (c) Implement the following Boolean function using a single 2×4 decoder with one-enable and active high outputs, and at most one logic gate.

$$G(A,B,C,D) = \sum m(2, 11)$$

The block diagram of a 2×4 decoder with one-enable and active high outputs is shown below.

[4 marks]

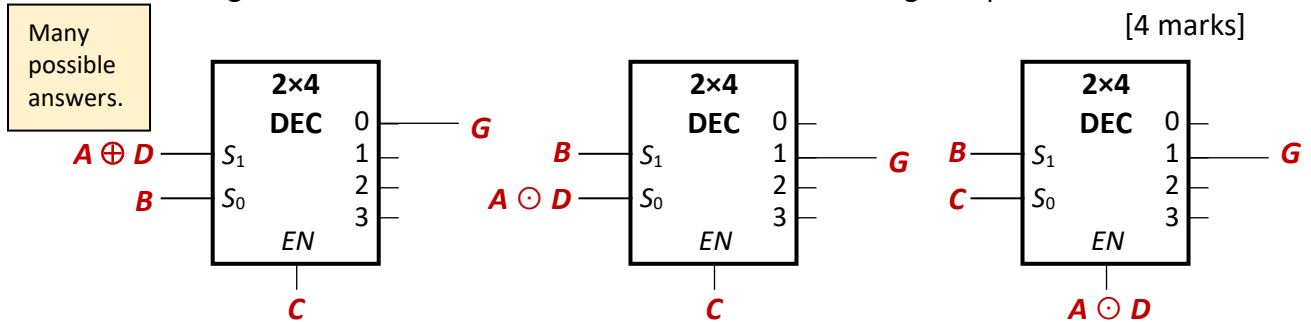

- (d) Below is a partial function table of an 8-to-3 priority encoder. It consists of 8 inputs (A_7 to A_0) and 3 outputs (F_2 to F_0). A_i has higher priority than A_j for $i > j$. The only invalid input combination occurs when all inputs are zeroes. 'X' represents don't-care.

Write out the simplified SOP expressions for F_2 , F_1 and F_0 .

[5 marks]

A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0	F_2	F_1	F_0
0	0	0	0	0	0	0	0	X	X	X
1	X	X	X	X	X	X	X	1	1	1
0	1	X	X	X	X	X	X	1	1	0
0	0	1	X	X	X	X	X	1	0	1
⋮								⋮		
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	0	0	1	0	0	0

Answer:


$$F_2 = A_7 + A_6 + A_5 + A_4$$

$$F_1 = A_7 + A_6 + A_5' \cdot A_4' \cdot A_3 + A_5' \cdot A_4' \cdot A_2$$


$$F_0 = A_7 + A_6' \cdot A_5 + A_6' \cdot A_4' \cdot A_3 + A_6' \cdot A_4' \cdot A_2' \cdot A_1$$

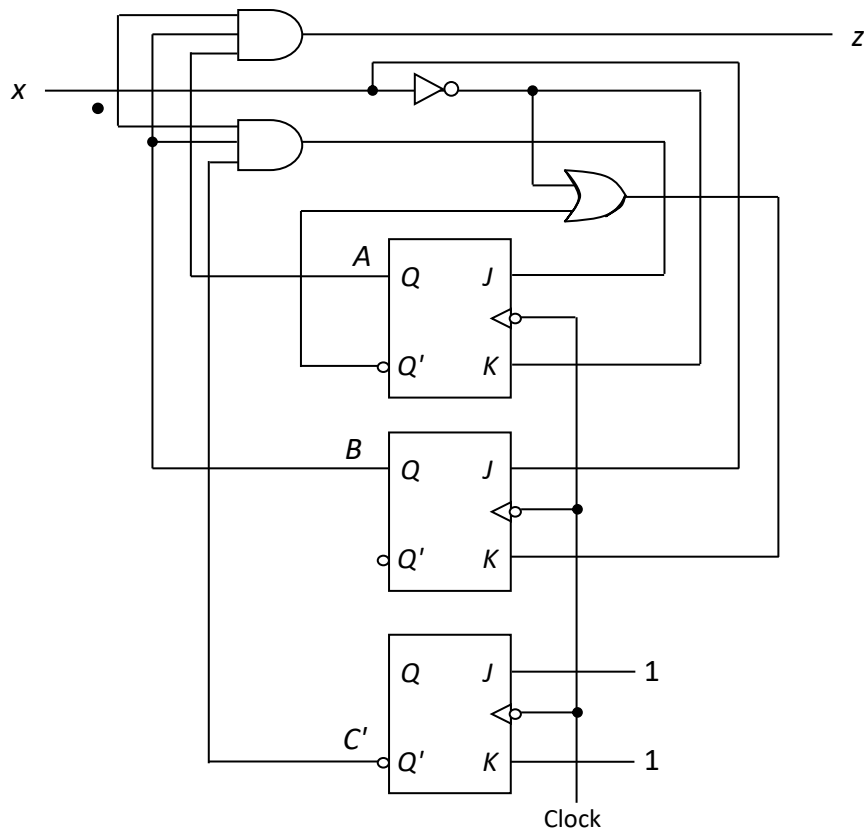Question 2. Sequential Circuits (14 marks)


Analyze the following sequential circuit with JK flip-flops, an input x and an output z . The states are represented by ABC .



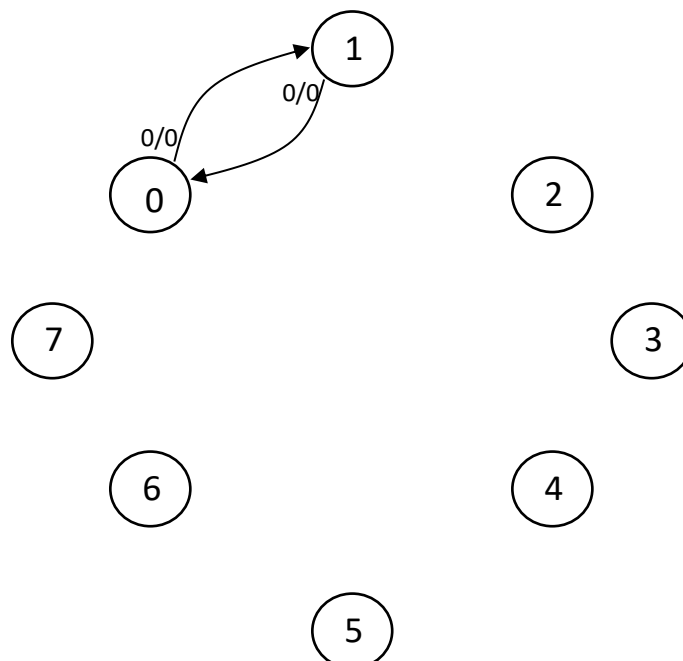Complete the state diagram for the circuit below. States are shown in decimal and the labels are in x/z format, where x is the input and z the output. Two arrows have been drawn for you. For ease of tracing, place a label near the start of its associated arrow. Use the same positions of the states in the diagram below to ease grading.



Answer:

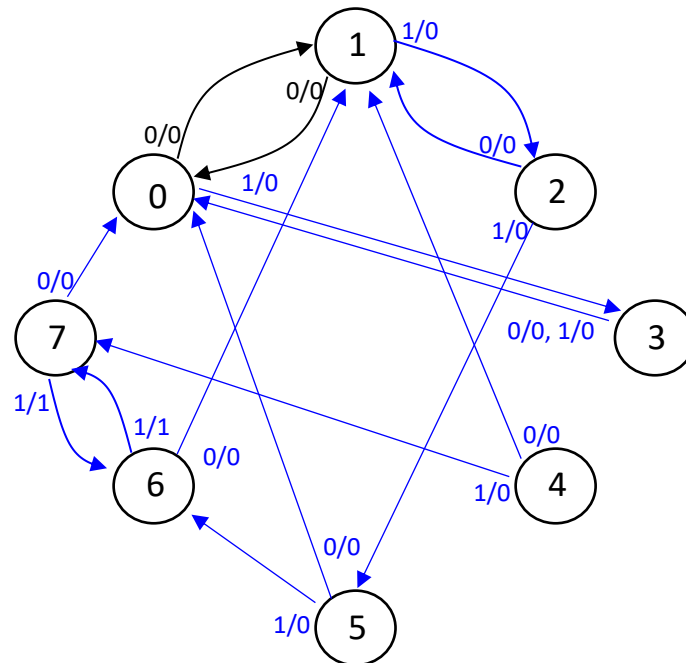

Working:

$$z = A \cdot B \cdot x; JA = B \cdot C' \cdot x; KA = x'; JB = x; KB = A' + x'; JC = KC = 1.$$

State table:

Present state			Input	Output	Flip-flop A		Flip-flop B		Flip-flop C		Next state		
A	B	C	x	z	JA	KA	JB	KB	JC	KC	A ⁺	B ⁺	C ⁺
0	0	0	0	0	0	1	0	1	1	1	0	0	1
0	0	0	1	0	0	0	1	1	1	1	0	1	1
0	0	1	0	0	0	1	0	1	1	1	0	0	0
0	0	1	1	0	0	0	1	1	1	1	0	1	0
0	1	0	0	0	0	1	0	1	1	1	0	0	1
0	1	0	1	0	1	0	1	1	1	1	1	0	1
0	1	1	0	0	0	1	0	1	1	1	0	0	0
0	1	1	1	0	0	0	1	1	1	1	0	0	0
1	0	0	0	0	0	1	0	1	1	1	0	0	1
1	0	0	1	0	0	0	1	0	1	1	1	1	1
1	0	1	0	0	0	1	0	1	1	1	0	0	0
1	0	1	1	0	0	0	1	0	1	1	1	1	0
1	1	0	0	0	0	1	0	1	1	1	0	0	1
1	1	0	1	1	1	0	1	0	1	1	1	1	1
1	1	1	0	0	0	1	0	1	1	1	0	0	0
1	1	1	1	1	0	0	1	0	1	1	1	1	0

Question 3. Pipelining (7 marks)

(Past year's exam question)

The following MIPS code reads an integer array **A**, whose base address is stored in **\$s0**, and computes some answer in **\$s2**. The register **\$s1** is associated with the integer variable **cutoff**.

	<code>addi \$s2, \$zero, 0</code>	# Inst1: <code>count = 0</code>
	<code>addi \$t0, \$s0, 40</code>	# Inst2: <code>\$t0 pts to A[10]</code>
		# <code>i = 9, 8, ..., 0</code>
Here:	<code>addi \$t0, \$t0, -4</code>	# Inst3: <code>\$t0 pts to A[i]</code>
	<code>lw \$t1, 0(\$t0)</code>	# Inst4: <code>\$t1 = A[i]</code>
	<code>slt \$t2, \$t1, \$s1</code>	# Inst5: <code>if (A[i] < cutoff)</code>
	<code>beq \$t2, \$zero, Skip</code>	# Inst6: {
	<code>addi \$s2, \$s2, 1</code>	# Inst7: <code>count++; }</code>
Skip:	<code>beq \$t0, \$s0, Fin</code>	# Inst8: <code>\$t0 pts to A[0]?</code>
	<code>j Here</code>	# Inst9
Fin:		

For parts (a) to (c) below, you are to calculate the total number of cycles required to complete the first iteration of the above code in a 5-stage MIPS pipeline, that is, instruction 1 through instruction 9. You need to count until the last stage (WB stage) of instruction 9. You may assume that all elements in array **A** have values that are smaller than **cutoff**.

- (a) In an ideal pipeline with no delays, how many cycles are needed to complete the first iteration of the code? (1 mark)
- (b) Assume without forwarding and branch is resolved at stage 4 (MEM) stage. No branch prediction is made and no delayed branching is used. What is the total number of cycles required to complete the first iteration of the code? (2 marks)
- (c) Assume with forwarding and branch is resolved at stage 2 (ID) stage. No branch prediction is made and no delayed branching is used. What is the total number of cycles required to complete the first iteration of the code? (2 marks)
- (d) For a general array (where the array elements have random values instead of all being smaller than **cutoff**), how would the choice of branch prediction (that is, choosing between "branch taken" and "branch not taken") affect the performance of this code with respect to the `beq` instruction in instruction 6? (2 marks)

Answers:

(a) Number of cycles = $9 + 5 - 1 = 13$.

(b) Number of cycles = 27.

Inst	Cycle																	
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18
1: addi	F	D	E	M	W													
2: addi		F	D	E	M	W												
3: addi			F	-	-	D	E	M	W									
4: lw				F	-	-	-	-	D	E	M	W						
5: slt					F	-	-	-	-	-	-	D	E	M	W			
6: beq						F	-	-	-	-	-	-	-	D	E	M	W	

Inst	Cycle												
	15	16	17	18	19	20	21	22	23	24	25	26	27
6: beq	D	E	M	W									
7: addi				F	D	E	M	W					
8: beq					F	D	E	M	W				
9: j									F	D	E	M	W

(c) Number of cycles = 17.

Inst	Cycle																	
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18
1: addi	F	D	E	M	W													
2: addi		F	D	E	M	W												
3: addi			F	D	E	M	W											
4: lw				F	D	E	M	W										
5: slt					F	D	-	E	M	W								
6: beq						F	-	-	D	E	M	W						
7: addi										F	D	E	M	W				
8: beq											F	D	E	M	W			
9: j													F	D	E	M	W	

(d) The choice of branch prediction will affect the performance of the code depending on how many array elements are smaller than the cut-off. If there are more array elements that are smaller than the cutoff, then “branch not taken” prediction would give a better performance. (Optionally: On the other hand, if there are more array elements that are larger than or equal to the cutoff, then “branch taken” prediction would give a better performance.) (2 marks)

=== END OF PAPER ===